

- (a) Upload the project report and netlist into Canvas. Filenames should be ECE522\_YourName/Names\_Project.pdf.
- (b) Further testbench instructions will be provided in class.
- (c) Project can be done alone or in a group of two.

You are required to design a two-stage single ended CMOS opamp with Miller (pole-splitting) compensation in the  $0.18\mu\text{m}$  process (the minimum channel length is  $0.18\mu\text{m}$ ). The parameters for this process are provided on Canvas. Your simulation results with the BSIM3 model must meet the specifications given below.

**The final report should be no longer than 3 pages of text.** Include a table comparing simulated results with the specifications. Attach all relevant analysis and simulations as appendices. If you are using hspice, you need to include AD/AS and PD/PS in your SPICE simulations. Assume  $AD = AS = 0.6\mu\text{m} \cdot W$ ,  $PD = PS = 1.2\mu\text{m} + 2 \cdot W$  where  $W$  is the transistor width in  $\mu\text{m}$ . The layout is not part of the project.

What is the simulated input common mode range (i.e.,  $V_{icmin}$  and  $V_{icmax}$ ) and output swing (i.e.,  $V_{o,max}$  and  $V_{o,min}$ ) for the designed opamp? Please make sure that the project report is concise and well documented.

Load capacitance	5pF
Power supply	Vdd = 0.9V, Vss = -0.9V
Open loop gain	$\geq 65dB$
Phase margin	$\geq 60^\circ$
Unity gain frequency	$\geq 15MHz$